

浙江大学

本科实验报告

课程名称: 计算机组成

姓 名: TANG ANNA YONGQI

学 院: 计算机科学与技术学院

专 业: 计算机科学与技术（中加班）留学生

学 号: 3180300155

生活照:



指导教师: 刘海风，洪奇军

2020 年 5 月 30 日

Lab 11 – Multicycle CPU Controller Design

Name: Anna Yongqi Tang

ID: 3180300155

Major: 计算机科学与技术（中加班）留学生

Course: Computer Organization

Date: 2020-05-30

Instructor: 洪奇军

1. Method and Experimental Steps

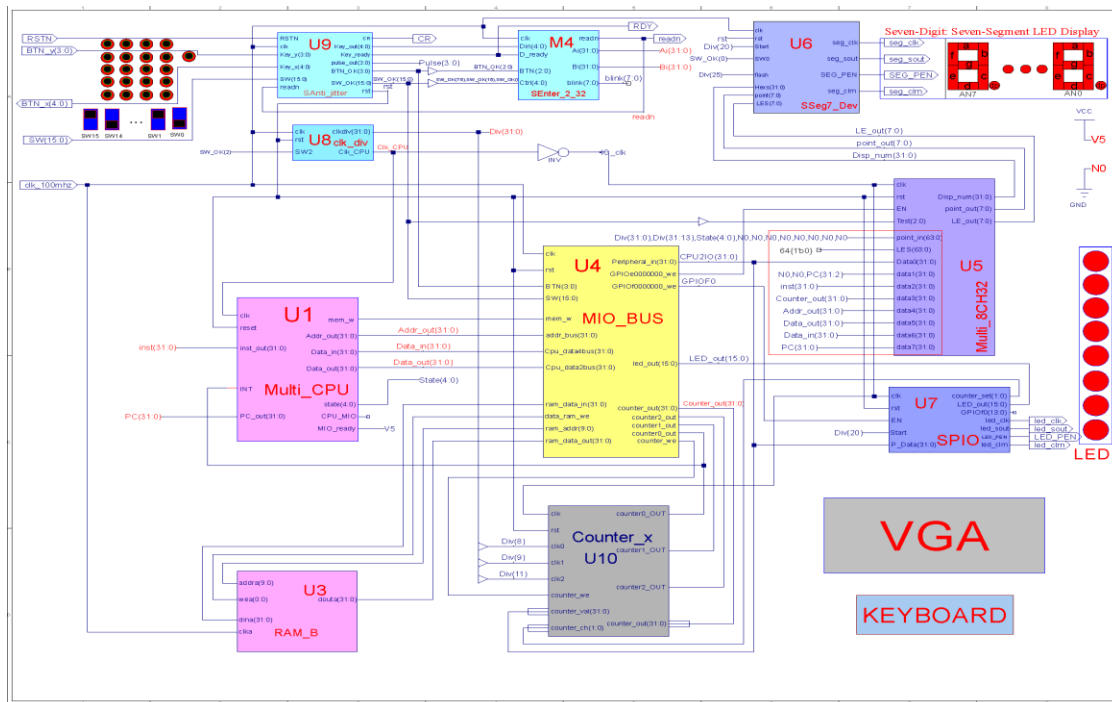


Figure 1 - topMod.sch

Lab 11 is a continuation of labs 9 and 1, which concentrate on a multicycle CPU implementation. before, an HDL implementation was used to implement the top module instead of the schematic pictured above. The main task of this experiment was to replace the Multi_CPU's controller ngc with an actual implementation. The .ucf for this program came from the provided courseware, and is linked to topMod.v. Synthesis had minimal warnings, and implementation was successful. A programmable file has been generated and is ready for testing on the SWORD board. The above diagram was retrieved from the lab PowerPoint. No schematic has been drawn for this experiment.

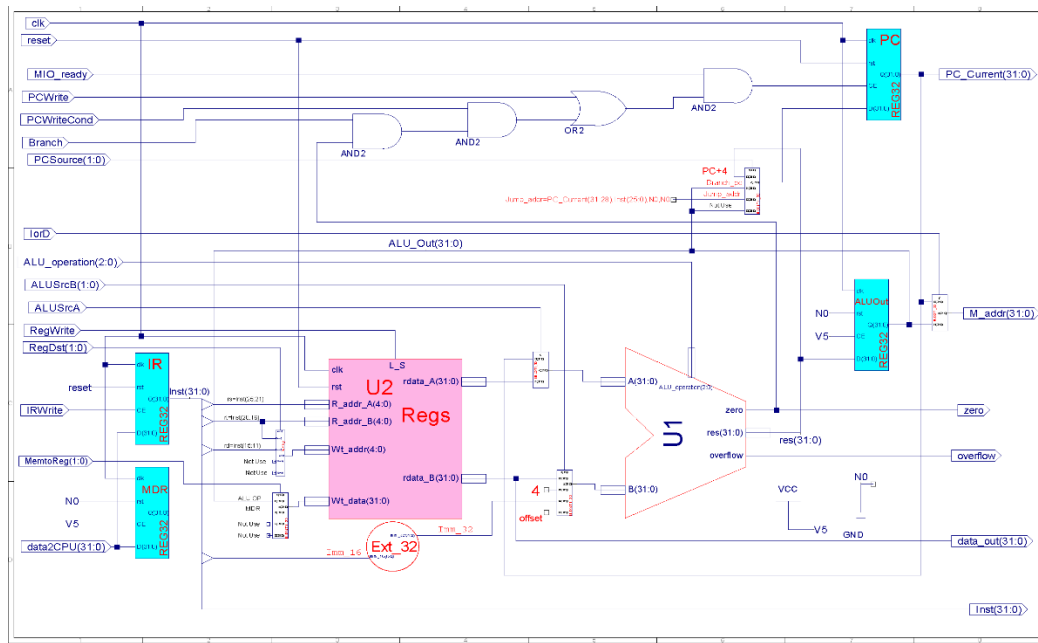


Figure 2 – M_datapath.sch

Instead of using the suggested schematic (pictured above), the M_datapath was constructed in HDL as well. This CPU currently supports 9 instructions: add, sub, and, or, slt, nor, lw, sw, beq and j. With the newly implemented controller, it sets the different controls for the instructions based on the FSM model. For each state/circle in the FSM, we define different value controls. The opcodes are also set accordingly in this module. After the controller finishes processing each module, it goes back to the instruction fetch stage.

 


Figure 3 – 3180300155_TANGANNAYONGQI_11

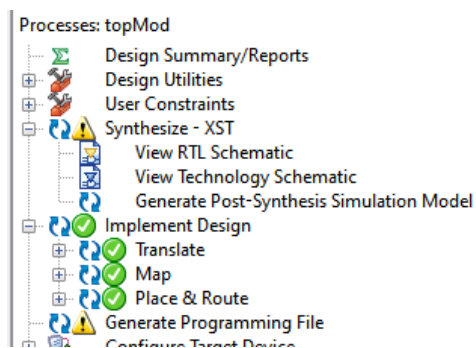


Figure 4 - .bit file generation



Figure 5 - .bit file generated in directory


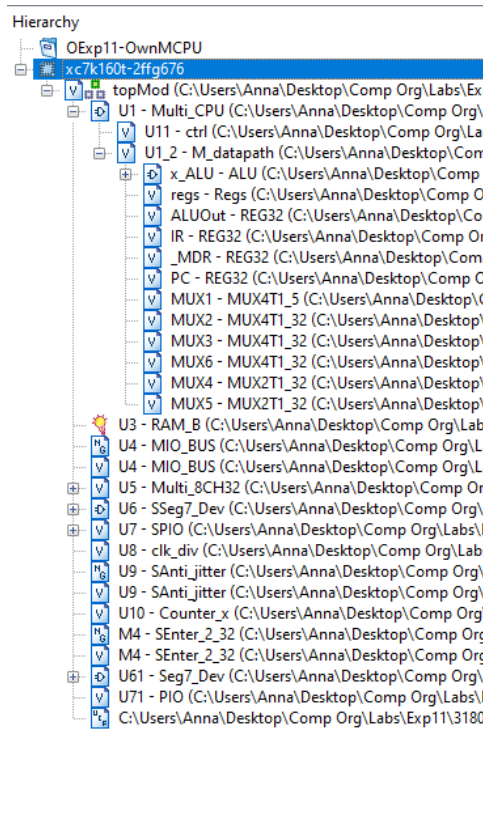


Figure 6 - file hierarchy

2. Simulations and Observations

This lab requires a MIPS program (MCPU_DEMO9.coe) to be tested on the multicyle CPU. The demo will be performed later in a future exercise. The controller module was simulated in this lab. Results seemed to be consistent with my predictions.

ctrl Simulation

 

ctrlSim.v

```
module ctrlSim;

    // Inputs
    reg clk;
    reg reset;
    reg [31:0] Inst_in;
    reg zero;
    reg overflow;
    reg MIO_ready;

    // Outputs
    wire MemRead;
    wire MemWrite;
    wire [2:0] ALU_operation;
    wire [4:0] state_out;
    wire CPU_MIO;
    wire IorD;
    wire IRWrite;
    wire [1:0] RegDst;
    wire RegWrite;
    wire [1:0] MemtoReg;
    wire ALUSrcA;
    wire [1:0] ALUSrcB;
    wire [1:0] PCSource;
    wire PCWrite;
    wire PCWriteCond;
    wire Branch;

    // Instantiate the Unit Under Test (UUT)
    ctrl uut (
        .clk(clk),
        .reset(reset),
        .Inst_in(Inst_in),
        .zero(zero),
        .overflow(overflow),
        .MIO_ready(MIO_ready),
        .MemRead(MemRead),
        .MemWrite(MemWrite),
        .ALU_operation(ALU_operation),
        .state_out(state_out),
        .CPU_MIO(CPU_MIO),
        .IorD(IorD),
        .IRWrite(IRWrite),
        .RegDst(RegDst),
        .RegWrite(RegWrite),
        .MemtoReg(MemtoReg),
        .ALUSrcA(ALUSrcA),
        .ALUSrcB(ALUSrcB),
        .PCSource(PCSource),
        .PCWrite(PCWrite),
        .PCWriteCond(PCWriteCond),
        .Branch(Branch)
    );

    initial begin
        // Initialize Inputs
```

```

        clk = 0;
        reset = 0;
        Inst_in = 0;
        zero = 0;
        overflow = 0;
        MIO_ready = 0;

        // Wait 100 ns for global reset to finish
        #50;
        reset=1;
        #60;
        reset=0;
        MIO_ready=1;
        Inst_in = 32'h014B4820; //add t1, t2, t3
        #50;
        Inst_in = 32'h2014003f; //addi s4, zero, 3f
        #50;
        Inst_in = 32'h11600005; //beq t3, zero, 5
        #50;
        Inst_in = 32'h0800000c; //j 12
        #50;
        Inst_in = 32'h00000000;
        #50;
    end

    always begin
        clk=0;
        #20;
        clk=1;
        #20;
    end
endmodule

```

3. Conclusion

This week's lab was an overview and a HDL implementation of the FSM model used to represent a multicycle CPU's controller unit. It reinforced the material that was taught in class, and it was interesting to see how a visual model would be represented in something more applicable like Verilog. As we are near completion of the Computer Organization labs, I look forward to completing the multicycle CPU.

4. Source Code

All modules and components were either retrieved from previous labs or directly taken from the given files.

Controller – multi_ctrl_IO.v

```

module ctrl(input  clk,
            input  reset,
            input  [31:0] Inst_in,
            input  zero,

```

```

        input  overflow,
        input  MIO_ready,
        output reg MemRead,
        output reg MemWrite,
        output reg[2:0]ALU_operation,
        output [4:0]state_out,

        output reg CPU_MIO,
        output reg IorD,
        output reg IRWrite,
        output reg [1:0]RegDst,
        output reg RegWrite,
        output reg [1:0]MementoReg,
        output reg ALUSrcA,
        output reg [1:0]ALUSrcB,
        output reg [1:0]PCSource,
        output reg PCWrite,
        output reg PCWriteCond,
        output reg Branch
    );

wire Rtype, LS, IBeq, Jump, Load, Store;
wire[5:0] OP = Inst_in[31:26];
reg[3:0] state;
reg[1:0] ALUOp;

parameter IF = 4'b0000, ID = 4'b0001, Mem_Ex = 4'b0010, Mem_RD = 4'b0011,
          LW_WB = 4'b0100, Mem_W = 4'b0101, R_Exc = 4'b0110, R_WB = 4'b0111,
          Beq_Exc = 4'b1000, J = 4'b1001, Error = 4'b1111;

`define Datapath_signals {PCWrite, PCWriteCond,IorD, MemRead, MemWrite,IRWrite, MementoReg,
PCSource, ALUSrcA, ALUSrcB, RegWrite, RegDst, Branch, ALUOp, CPU_MIO}

parameter value0 = 20'b1001010000000100000000, value1 = 20'b0000000000001100000000,
          value2 = 20'b0000000000011000000000, value3 = 20'b0011000000000000000001,
          value4 = 20'b0000000010000010000000, value5 = 20'b0010100000000000000001,
          value6 = 20'b000000000001000000100, value7 = 20'b00000000000001010000,
          value8 = 20'b01000000011000001010, value9 = 20'b10000000100000000000;

parameter AND=3'b000, OR=3'b001, ADD=3'b010, SUB=3'b110, NOR=3'b100, SLT=3'b111, XOR=3'b011,
          SRL=3'b101;

assign Rtype = ~|OP; //if OP=000000 then Rtype = 1
assign LS = (OP == 6'b10x011) ? 1 : 0; //if OP=10x011 then LS = 1
assign IBeq = (OP == 6'b000100) ? 1 : 0; //if OP=000100 then Ibeq = 1
assign Jump = (OP == 6'b000010) ? 1 : 0; //if OP=000010 then Jump = 1
assign Load = (OP == 6'b100011) ? 1 : 0; //if OP=100011 then Load = 1
assign Store = (OP == 6'b101011) ? 1 : 0; //if OP=101011 then Store = 1

always @ (posedge clk or posedge reset)
    if (reset==1) state <= IF;
    else
        case(state)
            IF: if(MIO_ready) state <= ID;
                else state <= IF;
            ID: case (Inst_in[31:26])
                    6'b000000: state <= R_Exc; //R-type OP
                    6'b100011: state <= Mem_Ex; //Lw
                    6'b101011: state <= Mem_Ex; //SW
                    6'b000100: state <= Beq_Exc; //beq
                    6'b000010: state <= J; //jump
                    default: state <= Error;
                endcase
            Mem_Ex: if(Inst_in[29]) state <= Mem_W;
                    else state <= Mem_RD;
            Mem_RD: state <= LW_WB;
        endcase

```

```

        LW_WB: state <= IF;
        Mem_W: state <= IF;
        R_Exc: state <= R_WB;
        R_WB: state <= IF;
        Beq_Exc: state <= IF;
        J: state <= IF;
        Error: state <= Error;
        default: state <= Error;
    endcase

always @ * begin
    case(state) //state
        IF: `Datapath_signals = value0;
        ID: `Datapath_signals = value1;
        Mem_Exc: `Datapath_signals = value2;
        Mem_RD: `Datapath_signals = value3;
        LW_WB: `Datapath_signals = value4;
        Mem_W: `Datapath_signals = value5;
        R_Exc: `Datapath_signals = value6;
        R_WB: `Datapath_signals = value7;
        Beq_Exc: `Datapath_signals = value8;
        J: `Datapath_signals = value9;
        default: `Datapath_signals = value0;
    endcase
end

always @ * begin
    case(ALUop)
        2'b00: ALU_operation = 3'b010; //add???
        2'b01: ALU_operation = 3'b110; //sub???
        2'b10:
            case (Inst_in[5:0])
                6'b100000: ALU_operation = ADD;
                6'b100010: ALU_operation = SUB;
                6'b100100: ALU_operation = AND;
                6'b100101: ALU_operation = OR;
                6'b100111: ALU_operation = NOR;
                6'b101010: ALU_operation = SLT;
                6'b000010: ALU_operation = SRL; //shfit 1bit right
                6'b000000: ALU_operation = XOR;
                default: ALU_operation = ADD;
            endcase
        2'b11: ALU_operation = 3'b111; //slti
    endcase
end

endmodule

```